

# Digital Communication Lab

Laboratory report submitted for the partial fulfillment  
of the requirements for the degree of

*Bachelor of Technology*  
*in*  
*Electronics and Communication Engineering*

by

Kartikeya Acharya 21uec072

Course Coordinator  
Dr. Nikhil Sharma



Department of Electronics and Communication Engineering  
The LNM Institute of Information Technology, Jaipur

September 2023

Copyright © The LNMIIT 2023  
All Rights Reserved

## Contents

Chapter	Page
1 Experiment - 09 .....	1
1.1 AIM .....	1
1.2 Apparatus Used.....	1
1.3 Theory .....	1
1.3.1 Circuit Diagram of PRBS Generator .....	1
1.3.2 Block Diagram of Clock Recovery .....	2
1.4 Results .....	2
1.4.1 Screenshot of PRBS signal and clock.....	2
1.4.2 Screenshot of PRBS signal and Multivibrator-1.....	3
1.4.3 Screenshot of PRBS signal and Multivibrator-2.....	3
1.4.4 Screenshot of PRBS signal and OR gate output .....	4
1.4.5 Screenshot of OR gate and BPF output .....	4
1.4.6 Screenshot of recovered signal and clock signal .....	5
1.4.7 Screenshot of recovered signal from NOT gate and clock signal .....	5
1.5 Conclusions .....	5
1.6 Precautions .....	5

## Chapter 1

### Experiment - 09

#### 1.1 AIM

- 1.Generation of PRBS Signal and recovery of the Clock.

#### 1.2 Apparatus Used

- |   |                      |                              |
|---|----------------------|------------------------------|
| 1. ICs: 74LS121 Mono Stable Multivibrator | 5. LM741 (Op - Amp)  | 9.LM393 (Voltage Comparator) |
| 2.74LS04 NOT Gate                         | 6. 74LS32 OR Gate    | 10. Connecting wires         |
| 3.DSO Probe                               | 7. Breadboard        | 11. Capacitor                |
| 4. Digital Storage Oscilloscope           | 8.Function Generator | 12.DC Power Supply           |

#### 1.3 Theory

##### 1.3.1 Circuit Diagram of PRBS Generator

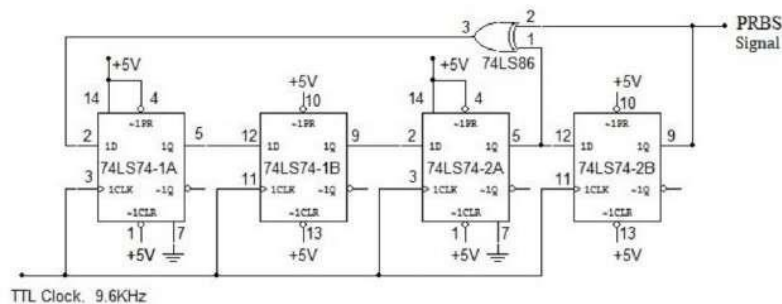


Figure 1: Circuit Diagram of PRBS Generator

### 1.3.2 Block Diagram of Clock Recovery

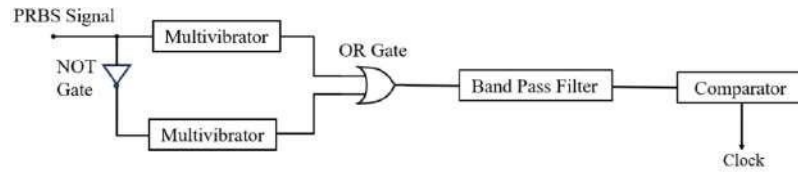


Figure 2: Block Diagram of Clock Recovery


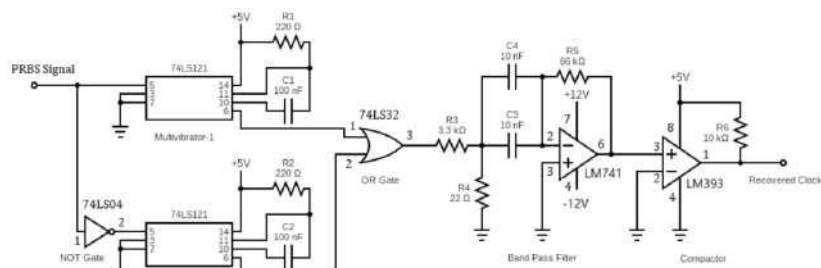



Figure 3: Circuit Diagram of Clock Recovery

## 1.4 Results

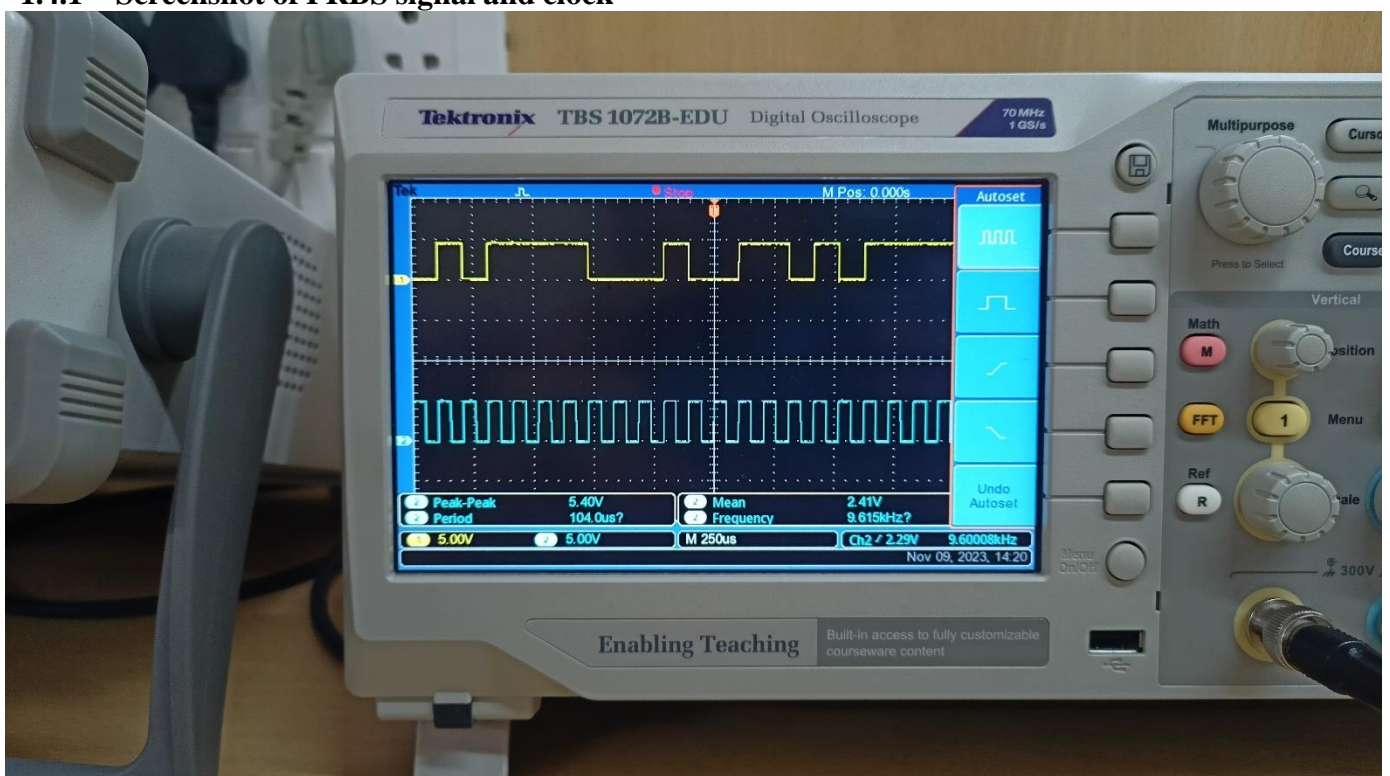
### 1.4.1 Screenshot of PRBS signal and clock


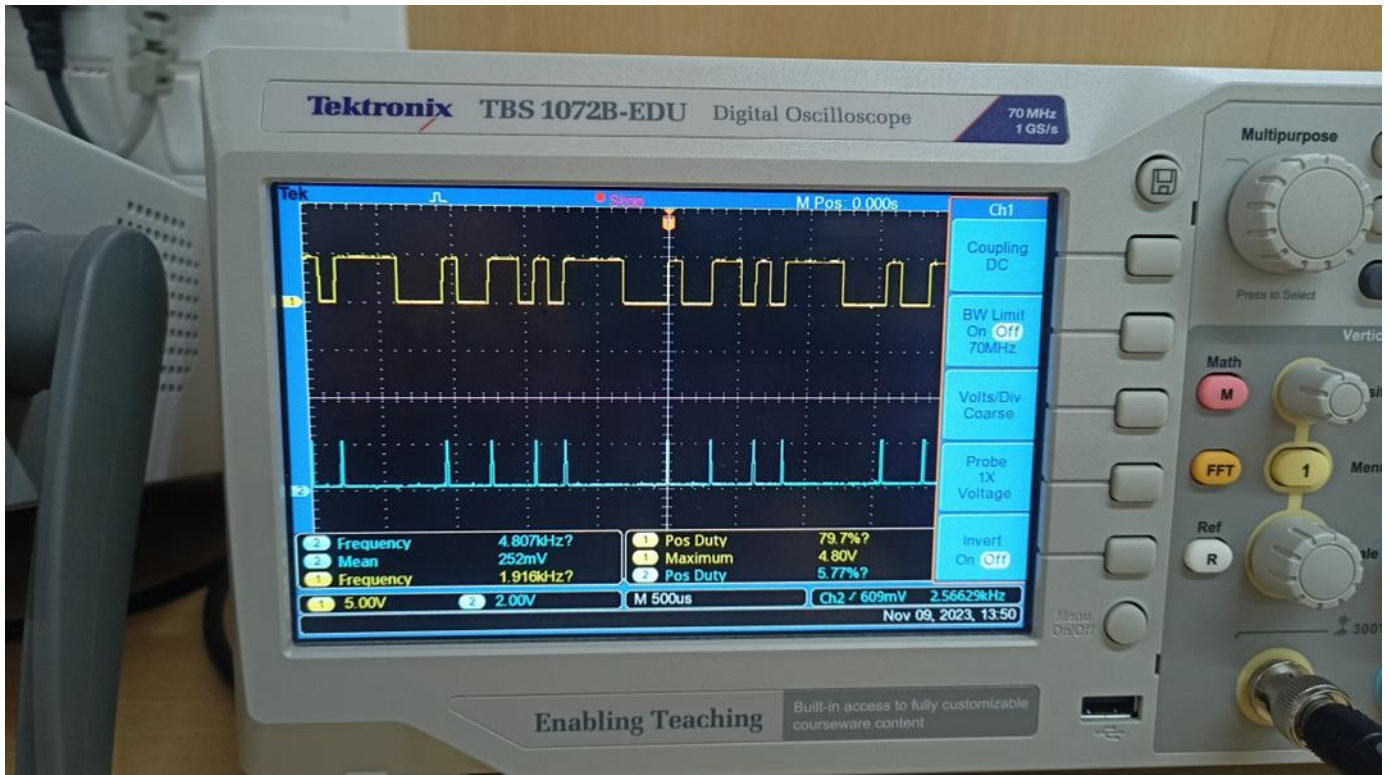
#### 1.4.2 Screenshot of PRBS signal and Multivibrator-1


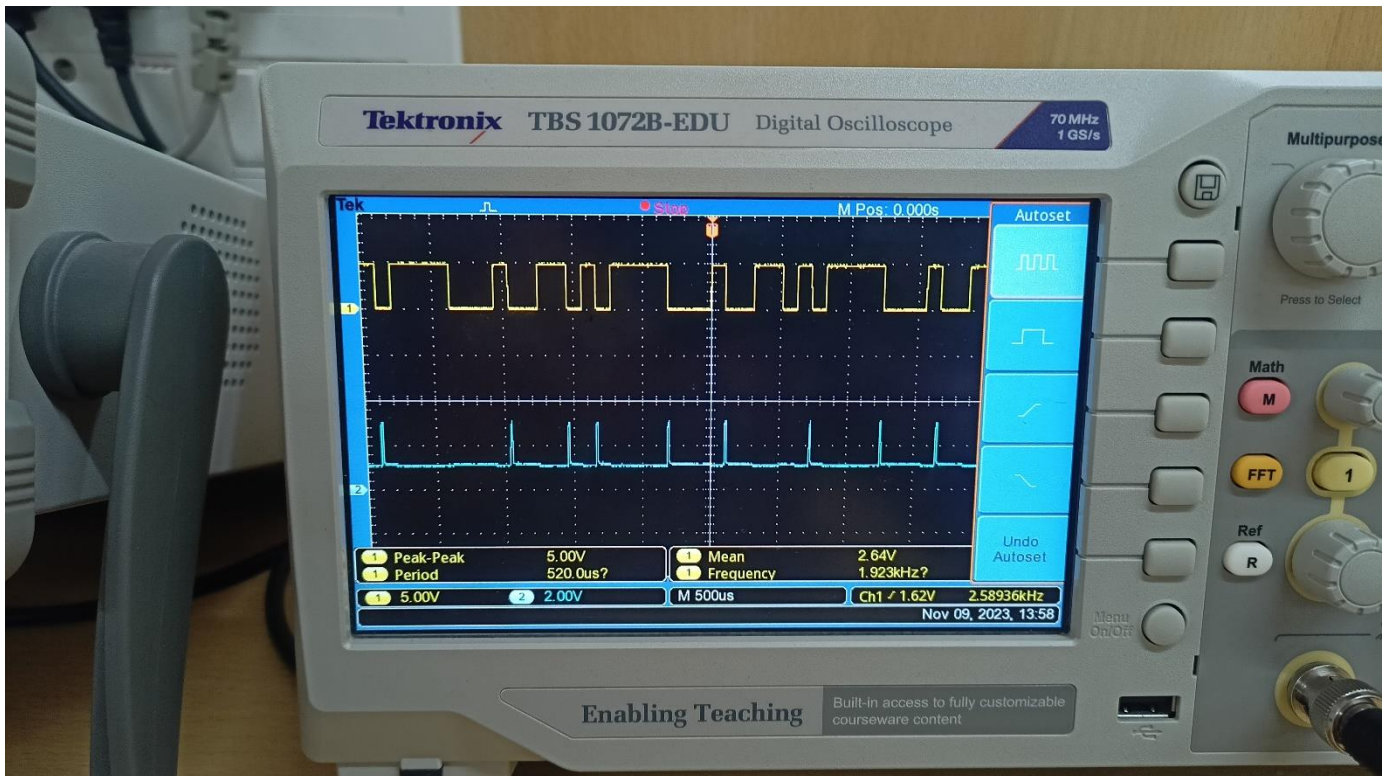
#### 1.4.3 Screenshot of PRBS signal and Multivibrator-2







#### 1.4.4 Screenshot of PRBS signal and OR gate output


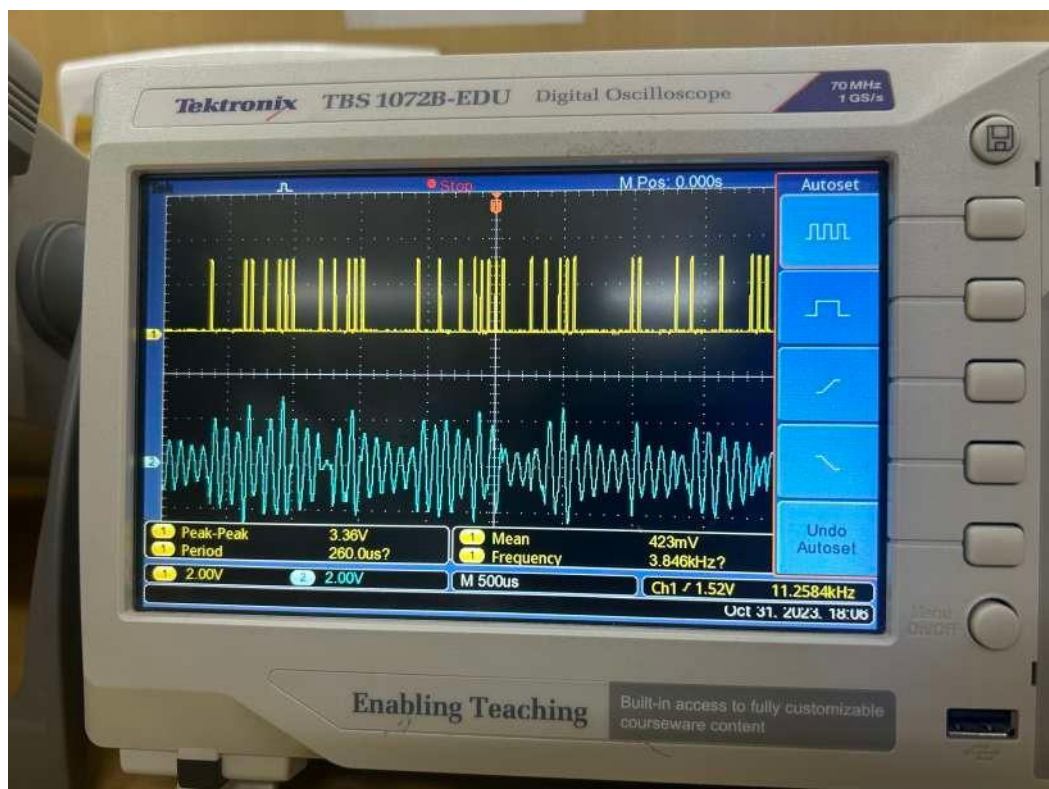
#### 1.4.5 Screenshot of OR gate and BPF output


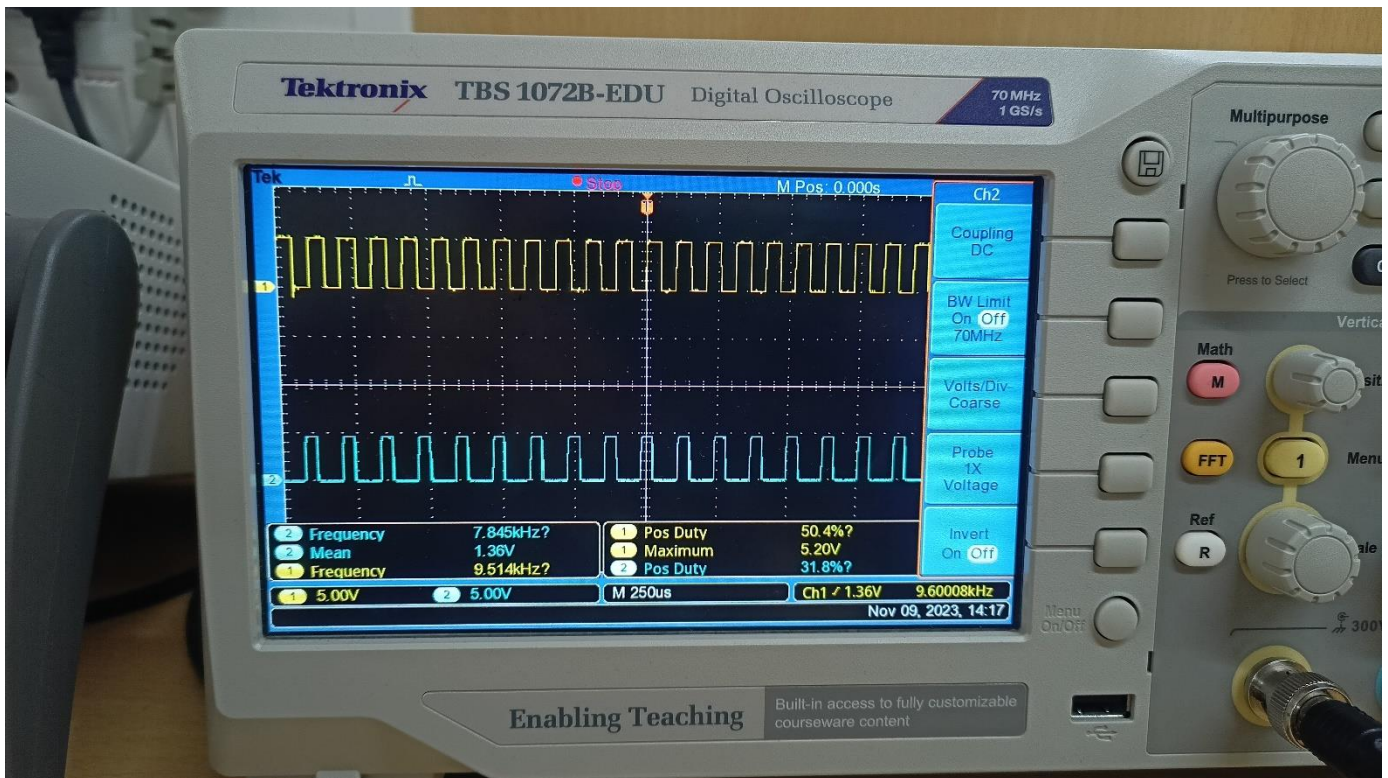
### 1.4.6 Screenshot of recovered signal and clock signal



## 1.5 Conclusions

1. From this experiment we learnt how to generate PRBS signal.
2. We learnt about the clock recovery after generation of PRBS signal.

## 1.6 Precautions

1. Check the connections before switching on the kit.
2. Connections should be done properly.
3. Observation should be taken properly.